

INTRODUCTION

The evolution of radio technology has been a cornerstone of modern communication, revolutionizing the way information and entertainment are disseminated. Among the various advancements in radio technology, Frequency Modulation (FM) receivers stand out for their ability to deliver high-quality sound with remarkable clarity and minimal interference. FM broadcasting, introduced by Edwin Armstrong in the 1930s, marked a significant improvement over the earlier Amplitude Modulation (AM) systems.

Principles of Frequency Modulation

Frequency Modulation (FM) involves varying the frequency of a carrier wave in direct proportion to the amplitude of the input signal, which typically represents audio information. Unlike AM, where the amplitude of the carrier wave is modulated while its frequency remains constant, FM maintains a constant amplitude and modulates the frequency. This fundamental difference endows FM with distinct advantages, including enhanced sound quality and improved resistance to noise and interference.

FM broadcasting operates within the Very High Frequency (VHF) band, specifically from 88 MHz to 108 MHz. This band is divided into channels, each occupying 200 kHz, allowing for multiple stations to coexist without significant overlap. The wider bandwidth allocated to FM channels enables the transmission of higher fidelity audio, making FM a preferred choice for music and high-quality voice broadcasts.

Components of an FM Receiver

An FM receiver is a complex system composed of several key components, each playing a crucial role in capturing, processing, and delivering the broadcast signal to the listener. The primary components include the antenna, RF tuner, mixer, intermediate frequency (IF) stage, demodulator, audio amplifier, and output transducer.

1. Antenna:

- The antenna is responsible for capturing FM signals from the air. It can range from simple whip antennas to more sophisticated dipole or Yagi antennas, designed to enhance signal reception and reduce multipath interference.

2. RF Tuner:

- The RF tuner selects the desired frequency from the myriad of signals captured by the antenna. It uses a combination of variable capacitors and inductors to tune to the specific frequency of the FM station.

3. Mixer:

- The mixer converts the selected RF signal to an intermediate frequency (IF), which is easier to process. This conversion is achieved by mixing the incoming RF signal with a locally generated signal, resulting in a new signal at the IF.

4. Intermediate Frequency (IF) Stage:

- The IF stage amplifies and filters the signal to improve its quality and prepare it for demodulation. Common IF frequencies for FM receivers are around 10.7 MHz, providing a balance between selectivity and ease of processing.

5. Demodulator:

- The demodulator extracts the original audio signal from the modulated carrier wave. Various demodulation techniques, such as the Foster-Seeley discriminator and phase-locked loop (PLL), are employed to achieve this task with high fidelity.

6. Audio Amplifier:

- The audio amplifier boosts the demodulated audio signal to a level suitable for driving speakers or headphones, ensuring that the sound is clear and loud enough for the listener.

7. Output:

- The final output stage delivers the amplified audio signal to the transducer, which can be speakers or headphones, completing the process of transforming electromagnetic waves into audible sound.

FM receivers represent a significant milestone in the history of radio technology, offering unparalleled sound quality and reliability. The principles of frequency modulation, combined with the sophisticated components of FM receivers, ensure that listeners receive clear, high-fidelity audio. As technology continues to advance, FM receivers remain a vital part of the broadcasting landscape, integrating seamlessly into a wide range of devices and applications.

Aim: To set up an FM receiver using an Audio Amplifier

Components required:


FM receiver (Built up FM Module):

1. IC cd1619cp.
2. Fixed Capacitors – 0.1uF, 1nF, 4.7nF, 20nF, 100nF, 4.7pF, 18pF, 22pF.
3. Variable Capacitors – 4.7mF, 100mF.
4. Resistors – 100 ohm, 270 ohm, 300 ohm, 100k ohm.

Audio Amplifier :

1. IC LM386.
2. Capacitors – 0.0478uF, 0.01uF, 10uF, 100uF, 220uF.
3. Resistors – 10 ohm, 10k ohm pot.
4. 16 ohm Speaker.

CIRCUIT :

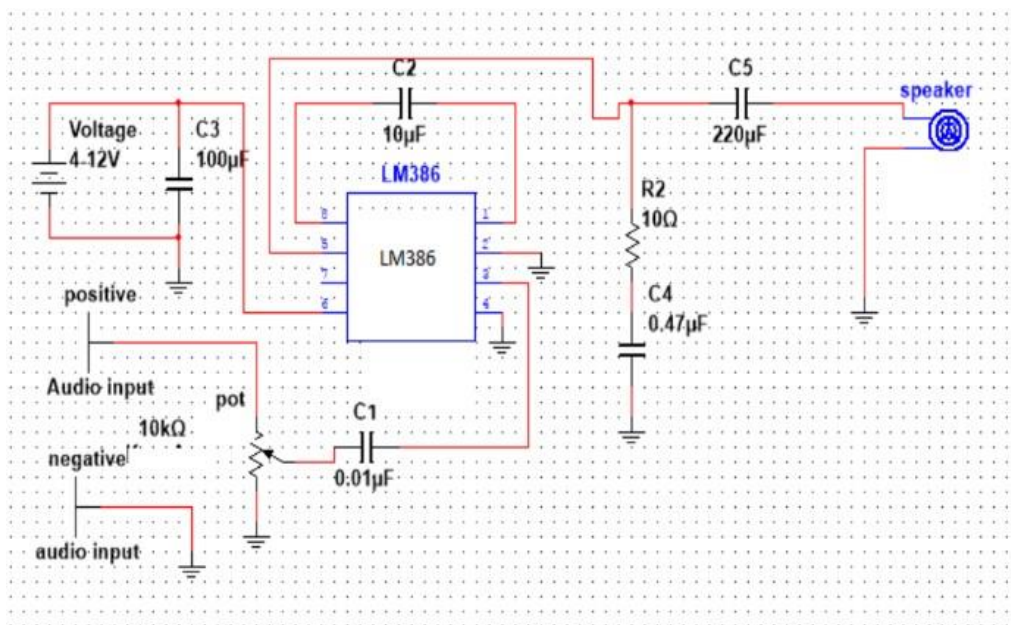

WORKING:

FM receivers are essential components in the landscape of radio communication, translating electromagnetic waves into audible sound. One effective way to design an FM receiver is by employing the CD1619 integrated circuit (IC) along with an audio amplifier. The CD1619 is a specialized IC that simplifies the process of demodulating frequency-modulated signals, making it a popular choice in FM receiver designs.

The FM receiver begins with an antenna that captures radio frequency (RF) signals from the air. These signals, typically in the range of 88 MHz to 108 MHz, represent the standard FM broadcast band. After capturing the signals, the RF tuner selects the desired FM station by tuning to its specific frequency. This tuning is achieved using a variable capacitor and inductor, which filter and amplify the selected RF signal, preparing it for further processing.

Radio broadcast transmitters are using the amplitude modulation on LW, MW and SW bandwidths. According to international treaties, each of the transmitters has a 9 kHz wide broadcasting channel, therefore making maximum frequency of the information being transferred $f_{NFmax}=4.5$ kHz, according to the characteristics of the AM signal. To put it more simple, the highest frequency of the sound that can be heard from the loudspeaker of an AM receiver is 4.5 kHz, all above it will be simply truncated in the circuitry.

The operation of an FM receiver using the CD1619 can be broken down into several key components and stages:

- **Antenna and RF Stage**
- **Mixer and IF Stage**
- **FM Demodulation**
- **Audio Pre-Amplifier**
- **Audio Amplifier**

- **Output**

The most important components are located below these 4.5 kHz (during the telephone transfer, all the components above 3.2 kHz are being cut, and nobody is complaining). Things stand different, however, for the transfer of music. Music has much more sound components, with their frequencies spreading up to 15 kHz, so truncating them above 4.5 kHz does deteriorate the transmission quality. The radio-broadcast FM transmitter has a 250 kHz wide channel on its disposal, therefore allowing for the maximum frequency of the information (acc. to the characteristics of the FM signal) to be $f_{NFmax}=15$ kHz. That means that music is being fully transferred and its quality is significantly better than in the case of the AM transfer. The FM transfer has some other advantages, perhaps the most significant of them being the possibility of eliminating various disturbances that are manifesting themselves as snapping, squeaking etc. The main disadvantage, however, is not the result of the frequency modulation itself, but rather of the fact that this method is being used on high frequencies, and that high-frequency electromagnetic waves behave themselves as light, spreading them in straight line, not reflecting from the ionosphere etc. This is why obtaining this kind of radio-link requires optical visibility between the transmission and reception antennas, which is not the case for the links obtained on frequencies which are less than 40 MHz.

